

Load Capacitance Measurement

One of the most commonly used crystal oscillation circuit nowadays is Pierce-gate as shown in figure 1. It comprises a simple inverter gate, a feedback resistor R_f , two external load capacitors C_a and C_b , and a crystal X_1 .

The equivalent circuit is shown in figure 2. At resonance, the crystal becomes a resistance RL in series with an inductance LL . The gate amplifier and its associated components form a negative resistance $-R$ in series with a load capacitance CL . According to Barkhausen criteria for oscillation, the reactance of LL would be exactly equal but opposite in sign to that of CL , and therefore the closed loop reactance becomes zero. In addition, the absolute magnitude of $-R$ ($|-R|$) must be greater than or equal to RL in order to have loop gain greater than or equal to unity. The ratio $|-R|/RL$ is called *oscillation allowance*. Higher oscillation allowance provides better safety margin when environment condition changed, such as temperature and humidity.

The equivalent circuit CL can be estimated by a simplified equation:

$$CL = \frac{(C_a + C_{in})(C_b + C_{out})}{C_a + C_{in} + C_b + C_{out}} + C_{stray} \quad (1)$$

where

C_{in} = internal pin capacitance of the gate input

C_{out} = internal pin capacitance of the gate output

C_{stray} = overall stray capacitance of the PCB

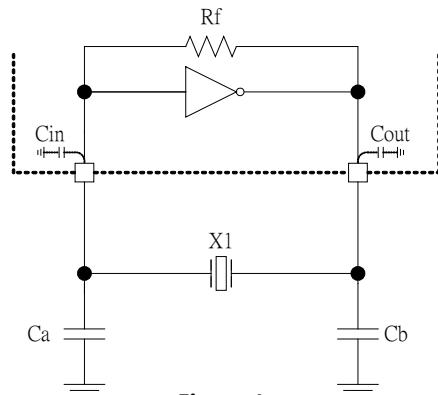


Figure 1

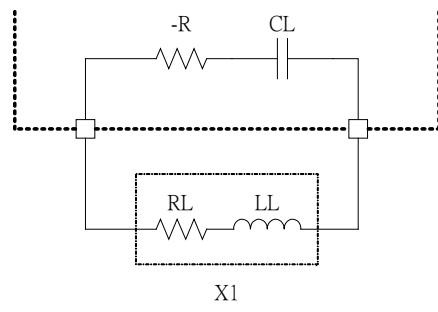


Figure 2

The above equation has been simplified with some assumption made, and should be used for rough estimation only. A more precise model would include the transconductance (gm) of the gate inverter, and also the C_0 of the crystal.

Another practical way to find CL is by using a crystal network analyzer and a spectrum analyzer. The circuit oscillating frequency f_{osc} would be picked up by non-contact hi-impedance probe (or antenna), and measured by a high precision spectrum analyzer with frequency accuracy at least 0.1ppm or better. Then the sample crystal would be removed from the PCB and measured with a precise crystal network analyzer. Measure the CL at which f_L equals f_{osc} . If an automatic crystal network analyzer is used (e.g. KOLINKER KH1800), the CL , C_0 , Rs and other crystal parameters could be measured automatically with compliance to IEC60444-11 international standard.

If an automatic crystal network analyzer is unavailable, the crystal parameters could also be measured with a general network analyzer. Please refer to the IEC60444 standard, or search "Direct Impedance Method" from the internet for details.